



Laboratory Report #8

Name: German E Felisarta III

Group Number: 3

Laboratory Exercise Title: Finite State Machines (FSMs)

Date Completed: 12/6/2020

Target Course Outcomes:

CO1: Create descriptions of digital hardware components such as in combinational and sequential circuits using synthesizable Verilog HDL constructs.

CO2: Verify the functionality of HDL-based components through design verification tools.

Exercise 8A:

In this exercise, a Moore FSM is made for a Binary/Gray Counter. The state diagram was first accomplished. After finishing the state diagram, the design entry was made based on it. Since it is a Moore FSM, it is relatively easy to create. The timing diagram outputs exactly what was expected or displayed on the State Diagram.

Fig 1a. State Diagram for Binary/Gray Counter

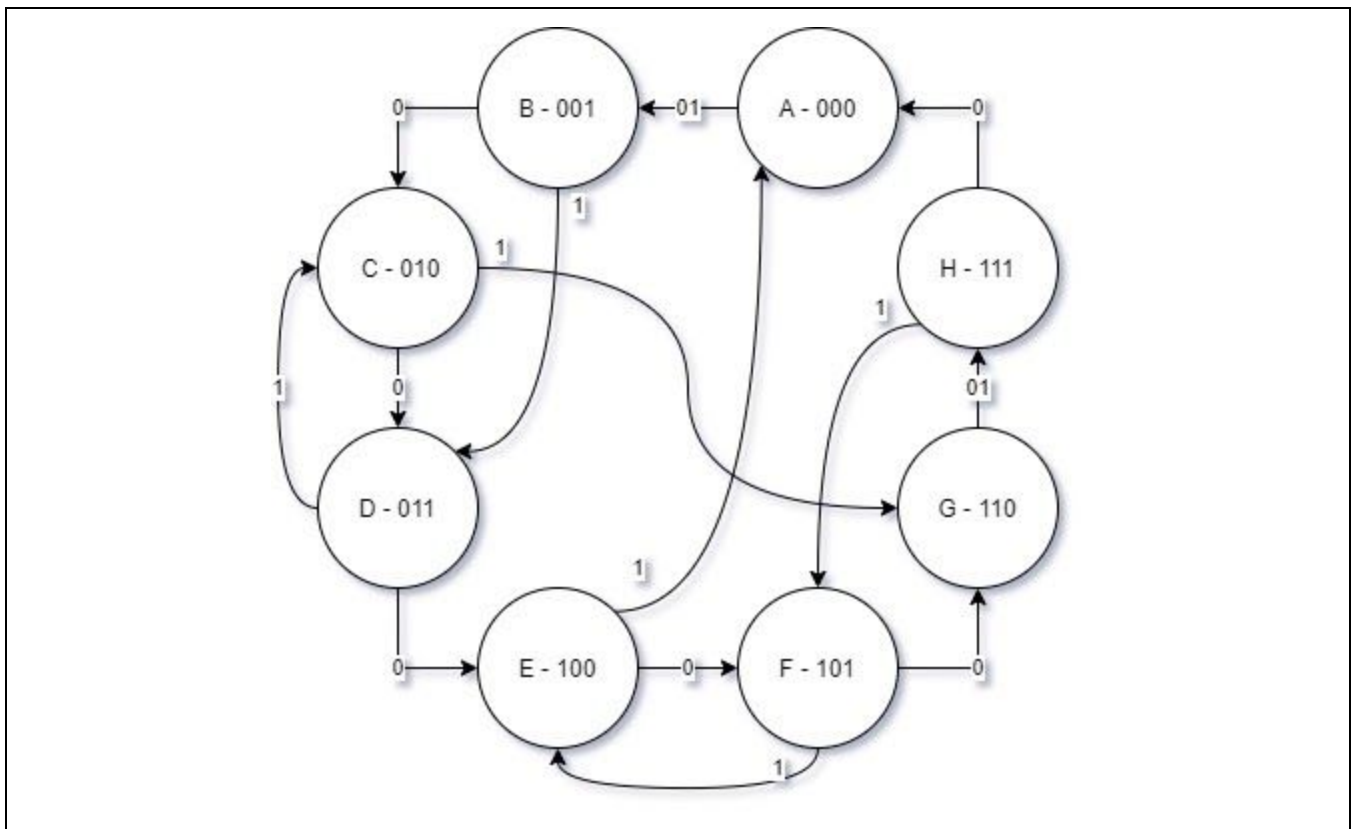




Fig 1b. Design Entry for Complex Counter

```
//German E Felisarta III 16101002 CpE 3101L Grp 3

module ComplexCounter(CLOCK, nReset, M, COUNT);

    input wire CLOCK, nReset, M;
    output reg [2:0]COUNT;

    parameter A = 3'b000;
    parameter B = 3'b001;
    parameter C = 3'b010;
    parameter D = 3'b011;
    parameter E = 3'b100;
    parameter F = 3'b101;
    parameter G = 3'b110;
    parameter H = 3'b111;
    reg [2:0]cstate, nstate;

    always @ (posedge CLOCK or negedge nReset)begin
        if (!nReset)
            cstate <= A;
        else
            cstate <= nstate;
    end

    always @ (*) begin
        case(cstate)
            A : nstate <= (M) ? B : B;
            B : nstate <= (M) ? D : C;
            C : nstate <= (M) ? G : D;
            D : nstate <= (M) ? C : E;
            E : nstate <= (M) ? A : F;
            F : nstate <= (M) ? E : G;
            G : nstate <= (M) ? H : H;
            default : nstate <= (M) ? F : A;
        endcase
    end

    always @ (*) begin
        COUNT <= cstate;
    end
endmodule
```



Fig 1c. Flow Summary for Complex Counter


Flow Summary	
<<Filter>>	
Flow Status	Successful - Fri Dec 04 18:10:00 2020
Quartus Prime Version	20.1.0 Build 711 06/05/2020 SJ Lite Edition
Revision Name	ComplexCounter
Top-level Entity Name	ComplexCounter
Family	MAX 10
Device	10M02DCU324A6G
Timing Models	Final
Total logic elements	11
Total registers	8
Total pins	6
Total virtual pins	0
Total memory bits	0
Embedded Multiplier 9-bit elements	0
Total PLLs	0
UFM blocks	0
ADC blocks	0

Fig 1d. Design Entry for Test Bench Complex Counter

```
1 //German E Felisarta III 16101002 CpE 3101L Grp 3
2
3 `timescale 1 ns / 1 ps
4 module tb_ComplexCounter ();
5
6     reg CLOCK, nReset, M;
7     wire [2:0]COUNT;
8
9     ComplexCounter UUT (CLOCK, nReset, M, COUNT);
10
11     initial CLOCK = 1'b0;
12
13     always #5 CLOCK = ~CLOCK;
14
15     initial begin
16
17         nReset = 1'b0; #20
18         nReset = 1'b1;
19
20     end
21
22     initial begin
23
24         M = 1'b0; #80
25         M = 1'b1; #80
26         M = 1'b0; #30
27         M = 1'b1; #20
28
29         $stop;
30
31     end
32 endmodule
```



Fig 1e. RTL Simulation for Complex Counter

 



Exercise 8B:

In this exercise, a Race Lights Controller is to be made, a Mealy FSM. First, the state diagram is made and the basis for input is the START variable. The output is the concatenation of RED, YELLOW, and GREEN variable outputs. The design entry was modeled after the State diagram. The timing diagram shows that it follows the expected output and displays the outputs projected by the state diagram.

Fig 2a. State Diagram for Race Lights Controller

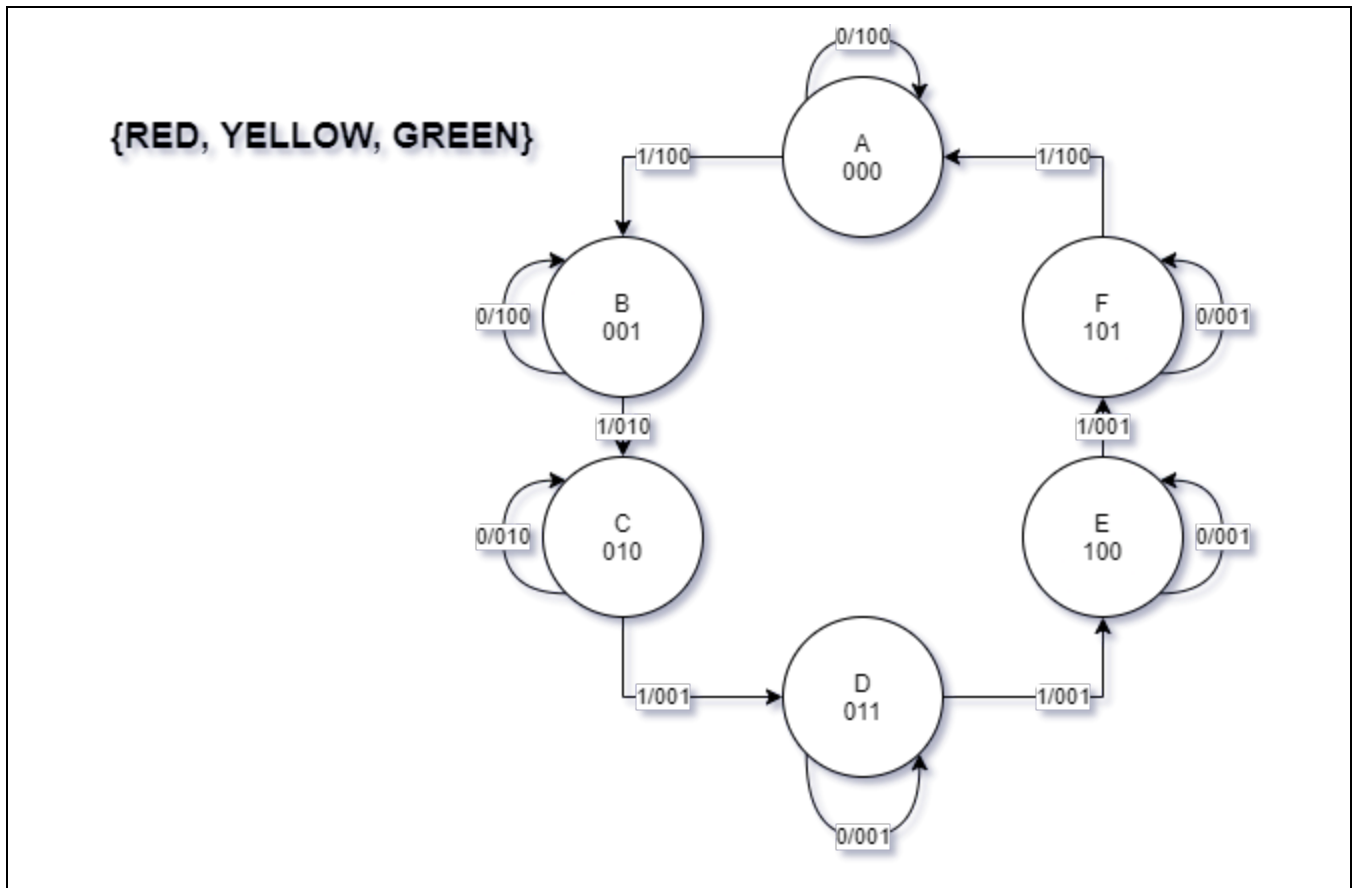




Fig 2b. Design Entry for Race Lights Controller

```
//German E Felisarta III 16101002      CpE 3101L Grp 3

module RaceLightsController(CLOCK, nReset, START, RED, YELLOW, GREEN);

    input wire CLOCK, nReset, START;
    output reg RED, YELLOW, GREEN;

    parameter R = 3'b100; //RED
    parameter Y = 3'b010; //YELLOW
    parameter G = 3'b001; //GREEN

    parameter A = 3'b000;
    parameter B = 3'b001;
    parameter C = 3'b010;
    parameter D = 3'b011;
    parameter E = 3'b100;
    parameter F = 3'b101;

    reg [2:0] cstate, nstate;
    reg [1:0] counter;//00, 01, 10

    always @ (posedge CLOCK or negedge nReset) begin

        if(!nReset)
            cstate <= A;
        else
            cstate <= nstate;

    end

    always @ (START, cstate) begin
        if (START) begin
            case(cstate)
                3'b000 : nstate <= B;
                3'b001 : nstate <= C;
                3'b010 : nstate <= D;
                3'b011 : nstate <= E;
                3'b100 : nstate <= F;
                default : nstate <= A;
            endcase
        end
    end

    always @ (*) begin
        case(cstate)
            3'b000 : {RED,YELLOW,GREEN} <= R;
            3'b001 : {RED,YELLOW,GREEN} <= Y;
            3'b010 : {RED,YELLOW,GREEN} <= G;
            3'b011 : {RED,YELLOW,GREEN} <= G;
            3'b100 : {RED,YELLOW,GREEN} <= G;
            3'b101 : {RED,YELLOW,GREEN} <= G;
```



```
                default: {RED,YELLOW,GREEN} <= R;  
            endcase  
        end  
    endmodule
```

Fig 2c. Flow Summary for Race Lights Controller


Flow Summary	
<<Filter>>	
Flow Status	Successful - Sun Dec 06 21:18:18 2020
Quartus Prime Version	20.1.0 Build 711 06/05/2020 SJ Lite Edition
Revision Name	RaceLightsController
Top-level Entity Name	RaceLightsController
Family	MAX 10
Device	10M02DCU324A6G
Timing Models	Final
Total logic elements	8
Total registers	6
Total pins	6
Total virtual pins	0
Total memory bits	0
Embedded Multiplier 9-bit elements	0
Total PLLs	0
UFM blocks	0
ADC blocks	0



Fig 2d. Design Entry for Test Bench Race Lights Controller

```
1 //GERMAN E FELISARTA III 16101002 CpE 3101L Grp 3
2
3 `timescale 1 ns / 1 ps
4 module tb_RaceLightsController();
5
6     reg CLOCK, nReset, START;
7     wire RED, YELLOW, GREEN;
8
9     RaceLightsController UUT (CLOCK, nReset, START, RED, YELLOW, GREEN);
10
11     initial CLOCK = 1'b0;
12
13     always #5 CLOCK = ~CLOCK;
14
15     initial begin
16         nReset = 1'b0; #10;
17         nReset = 1'b1;
18     end
19
20     initial begin
21         START = 1'b1; #70;
22         $stop;
23     end
24
25 endmodule
```

Fig 2e. RTL Simulation for Race Lights Controller

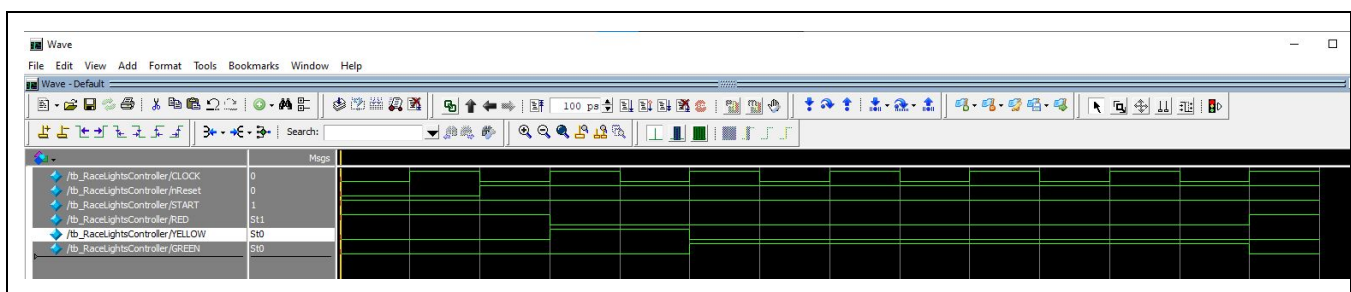



Exercise 8C:

In this exercise, a Washing Machine Controller is to be made, a Moore FSM was used. First, the state diagram is made and the basis for input are MEDIUM, LARGE, DIRTY, WET, T1Done, and T2Done. The output is the concatenation of MEDIUM, LARGE, WASH, RINSE, DRY, T1Start, and T2Start variable outputs. The design entry was modeled after the State diagram. The timing diagram shows that it follows the expected output but only up to STATE C, the design cannot reach other states. The experiment is unsuccessful.

Fig 3a. State Diagram for Washing Machine

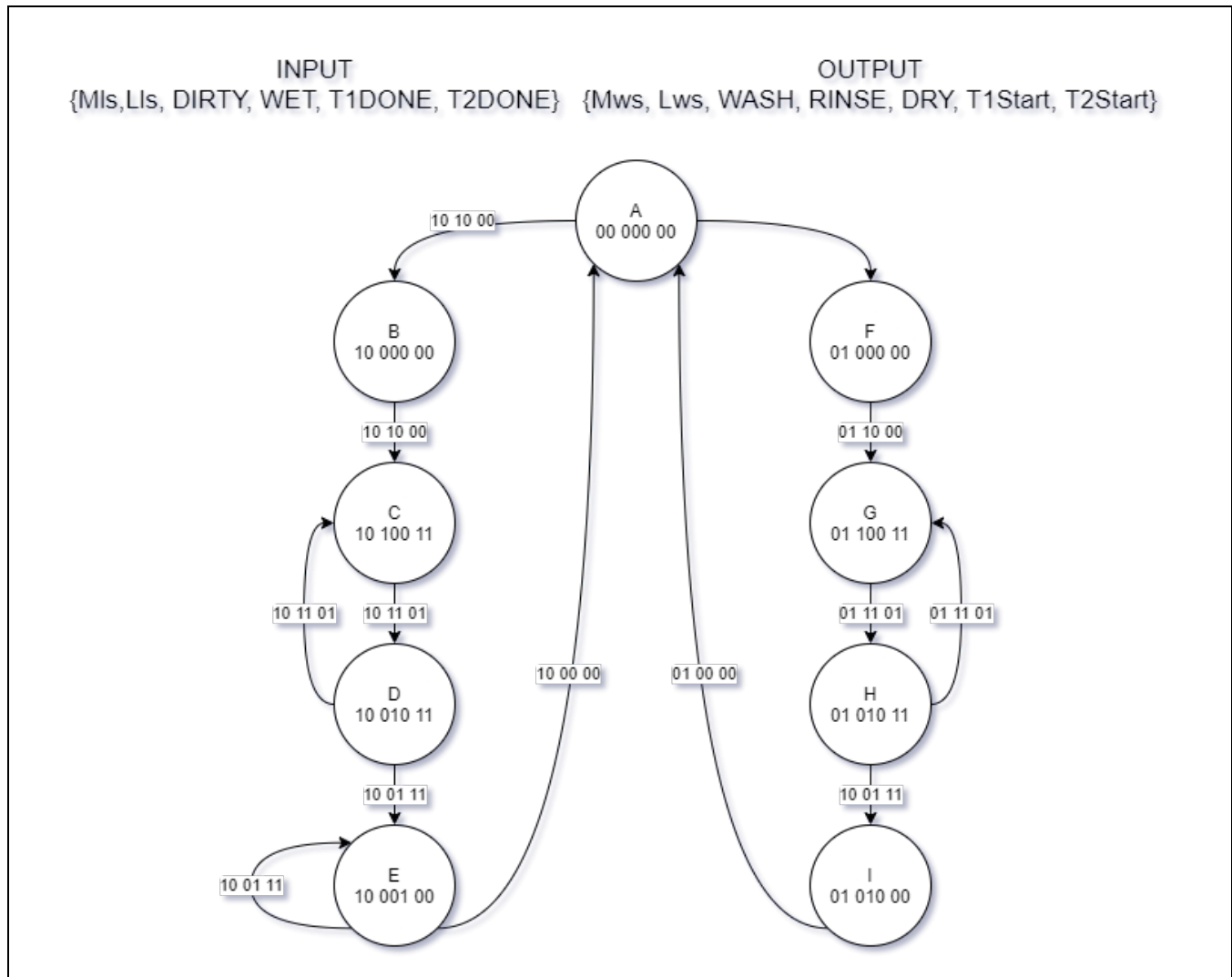




Fig 3b. Design Entry for Washing Machine

```
//German E Felisarta III 16101002      CpE 3101L Grp 3

module WashingMachineController(CLOCK, nReset, START, MIs, LIs, DIRTY, WET, T1Done, T2Done, Mws,
Lws, WASH, RINSE, DRY, T1Start, T2Start);

    input wire CLOCK, nReset, START, MIs, LIs, DIRTY, WET, T1Done, T2Done;
    output reg Mws, Lws, WASH, RINSE, DRY, T1Start, T2Start;

    //INPUTS
    //CLOCK, nReset
    //START
    //{MIs,LIs, DIRTY, WET, T1DONE, T2DONE}

    //OUTPUTS
    //{Mws, Lws, WASH, RINSE, DRY, T1Start, T2Start}

    reg [6:0]cstate, nstate;
    reg [2:0]counter;

    parameter A = 7'b00000000;
    parameter B = 7'b10000000;
    parameter C = 7'b10100111;
    parameter D = 7'b10010111;
    parameter E = 7'b10001000;
    parameter F = 7'b01000000;
    parameter G = 7'b01100111;
    parameter H = 7'b01010111;
    parameter I = 7'b01010000;

    always @ (posedge CLOCK or negedge nReset)begin

        if(!nReset)
            cstate <= A;
        else
            cstate <= nstate;

    end

    always @ (*) begin

    if (START) begin

    case(cstate)
        A : nstate <= ({MIs,LIs, DIRTY, WET, T1Done, T2Done} == 6'b101000) ? B : F;
        B : nstate <= ({MIs,LIs, DIRTY, WET, T1Done, T2Done} == 6'b101000) ? C : B;
        C : nstate <= ({MIs,LIs, DIRTY, WET, T1Done, T2Done} == 6'b101101) ? D : C;

        D : begin
            if({MIs,LIs, DIRTY, WET, T1Done, T2Done} == 6'b100111) nstate <= E;
            else if({MIs,LIs, DIRTY, WET, T1Done, T2Done} == 6'b101101) nstate <= C;
        end
    end

    end
```



```
E : begin
    if({Mls,Lls, DIRTY, WET, T1Done, T2Done} == 6'b100000) nstate <= A;
    else if({Mls,Lls, DIRTY, WET, T1Done, T2Done} == 6'b100111) nstate <= E;
end

F : nstate <= ({Mls,Lls, DIRTY, WET, T1Done, T2Done} == 6'b011000) ? G : F;
G : nstate <= ({Mls,Lls, DIRTY, WET, T1Done, T2Done} == 6'b011101) ? H : G;
H : begin
    if({Mls,Lls, DIRTY, WET, T1Done, T2Done} == 6'b010111) nstate <= I;
    else if({Mls,Lls, DIRTY, WET, T1Done, T2Done} == 6'b011101) nstate <= G;
end

I : begin
    if({Mls,Lls, DIRTY, WET, T1Done, T2Done} == 6'b010111) nstate <= I;
    else if({Mls,Lls, DIRTY, WET, T1Done, T2Done} == 6'b010000) nstate <= A;
end

endcase
end
end

always @ (*)
    {Mws, Lws, WASH, RINSE, DRY, T1Start, T2Start} <= cstate;

endmodule
```



Fig 3c. Flow Summary for Washing Machine

The screenshot shows the 'Flow Summary' window in Quartus Prime. The window title bar includes 'troller.v', 'tb_WashingMachineController.v', and 'Compilation Report - Wa'. The 'Flow Summary' tab is active, displaying a table of compilation statistics. The table has two columns: the metric name and its value. The metrics include Flow Status (Successful), Quartus Prime Version (20.1.0), Revision Name (WashingMachineController), Top-level Entity Name (WashingMachineController), Family (MAX 10), Device (10M02DCU324A6G), Timing Models (Final), and various resource counts like Total logic elements (43), Total registers (9), Total pins (16), Total virtual pins (0), Total memory bits (0), Embedded Multiplier 9-bit elements (0), Total PLLs (0), UFM blocks (0), and ADC blocks (0).

Metric	Value
Flow Status	Successful - Sun Dec 06 20:47:10 2020
Quartus Prime Version	20.1.0 Build 711 06/05/2020 SJ Lite Edition
Revision Name	WashingMachineController
Top-level Entity Name	WashingMachineController
Family	MAX 10
Device	10M02DCU324A6G
Timing Models	Final
Total logic elements	43
Total registers	9
Total pins	16
Total virtual pins	0
Total memory bits	0
Embedded Multiplier 9-bit elements	0
Total PLLs	0
UFM blocks	0
ADC blocks	0

Fig 3d. Design Entry for Test Bench Washing Machine

```
//German E Felisarta III 16101002      CpE 3101L Grp 3

`timescale 1 ns / 1 ps
module tb_WashingMachineController();

    reg CLOCK, nReset, START, MIs, LIs, DIRTY, WET, T1Done, T2Done;
    wire Mws, Lws, WASH, RINSE, DRY, T1Start, T2Start;

    WashingMachineController UUT (CLOCK, nReset, START, MIs, LIs, DIRTY, WET, T1Done, T2Done,
    Mws, Lws, WASH, RINSE, DRY, T1Start, T2Start);

    initial CLOCK = 1'b0;

    always #5 CLOCK = ~CLOCK;

    initial begin
```



```
        nReset = 1'b0; #10
        nReset = 1'b1;
    end

    initial begin
        START = 1'b0; #10
        START = 1'b1;
    end

    initial begin
        {Mls,Lls, DIRTY, WET, T1Done, T2Done} = 6'b101000;#15 // @A going B
        {Mls,Lls, DIRTY, WET, T1Done, T2Done} = 6'b101000;#15 // @B going C
        {Mls,Lls, DIRTY, WET, T1Done, T2Done} = 6'b101101;#15 // @C going D   #1
        {Mls,Lls, DIRTY, WET, T1Done, T2Done} = 6'b101101;#15 // @D going C
        {Mls,Lls, DIRTY, WET, T1Done, T2Done} = 6'b101101;#15 // @C going D   #2
        {Mls,Lls, DIRTY, WET, T1Done, T2Done} = 6'b101101;#15 // @D going C
        {Mls,Lls, DIRTY, WET, T1Done, T2Done} = 6'b101101;#15 // @C going D   #3
        {Mls,Lls, DIRTY, WET, T1Done, T2Done} = 6'b100111;#15 // @D going E
        {Mls,Lls, DIRTY, WET, T1Done, T2Done} = 6'b100111;#15 // @E first loop to 20Mins
        {Mls,Lls, DIRTY, WET, T1Done, T2Done} = 6'b100000;#10 // @E going A

        {Mls,Lls, DIRTY, WET, T1Done, T2Done} = 6'b011000;#15 // @A going F
        {Mls,Lls, DIRTY, WET, T1Done, T2Done} = 6'b011000;#15 // @F going G
        {Mls,Lls, DIRTY, WET, T1Done, T2Done} = 6'b011101;#15 // @G going H   #1
        {Mls,Lls, DIRTY, WET, T1Done, T2Done} = 6'b011101;#15 // @H going G
        {Mls,Lls, DIRTY, WET, T1Done, T2Done} = 6'b011101;#15 // @G going H   #2
        {Mls,Lls, DIRTY, WET, T1Done, T2Done} = 6'b011101;#15 // @H going G
        {Mls,Lls, DIRTY, WET, T1Done, T2Done} = 6'b011101;#15 // @G going H   #3
        {Mls,Lls, DIRTY, WET, T1Done, T2Done} = 6'b010111;#15 // @H going I
        {Mls,Lls, DIRTY, WET, T1Done, T2Done} = 6'b010111;#15 // @I first loop to 20Mins
        {Mls,Lls, DIRTY, WET, T1Done, T2Done} = 6'b010000;#15 // @I going A

        $stop;
    end

endmodule
```

Fig 3e. RTL Simulation for Washing Machine

