



Laboratory Report #2

Name: German E Felisarta III

Group Number: 3

Laboratory Exercise Title: Basic Constructs in Verilog HDL

Date Completed: 09-27-2020

Target Course Outcomes:

CO1: Create descriptions of digital hardware components such as in combinational and sequential circuits using synthesizable Verilog HDL constructs.


CO2: Verify the functionality of HDL-based components through design verification tools.

Exercise 2A:

In exercise 2A, that task was to setup the testbench of the halfadder circuit. First, the ModelSim-Altera feature of the Quartus Software was setup, then the design entry was coded to program how the simulation will run, it has 2 inputs that explains the variables x and y which were treated as regs, and 2 outputs, C and S which were treated as wire types. The design entry/code can be found on Figure 1.1 After writing the testbench code, it was added to the group of testbench for the ModelSim-Altera.

After setting-up the testbench, the project was analyzed and synthesized, flow summary can be found in Figure 1.23. Then after, the RTL Simulation with framework ModelSim-Altera was run. In the RTL Simulation, the timing diagram of the outputs were displayed as seen on Figure 1.3.

Figure 1.1. Design Entry of Test Bench

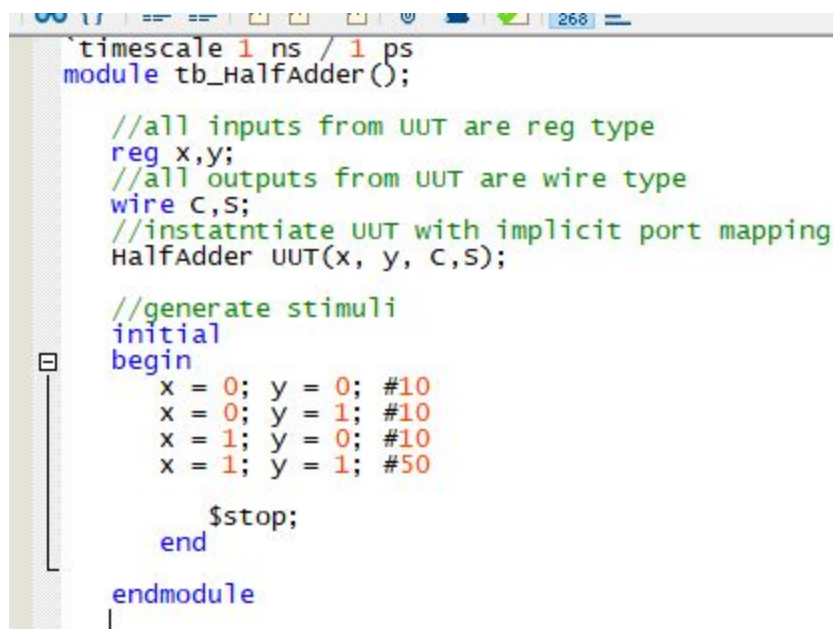

```
timescale 1 ns / 1 ps
module tb_HalfAdder();

    //all inputs from UUT are reg type
    reg x,y;
    //all outputs from UUT are wire type
    wire C,S;
    //instantiate UUT with implicit port mapping
    HalfAdder UUT(x, y, C,S);

    //generate stimuli
    initial
    begin
        x = 0; y = 0; #10
        x = 0; y = 1; #10
        x = 1; y = 0; #10
        x = 1; y = 1; #50


        $stop;
    end
endmodule
```



Figure 1.2. Flow Summary

Flow Summary	
<<Filter>>	
Flow Status	Successful - Wed Sep 23 10:35:02 2020
Quartus Prime Version	20.1.0 Build 711 06/05/2020 SJ Lite Edition
Revision Name	HalfAdder
Top-level Entity Name	HalfAdder
Family	MAX 10
Device	10M50DCF484C7G
Timing Models	Final
Total logic elements	2
Total registers	0
Total pins	4
Total virtual pins	0
Total memory bits	0
Embedded Multiplier 9-bit elements	0
Total PLLs	0
UFM blocks	0
ADC blocks	0

Figure 1.3. Timing Diagram in ModelSim-Altera

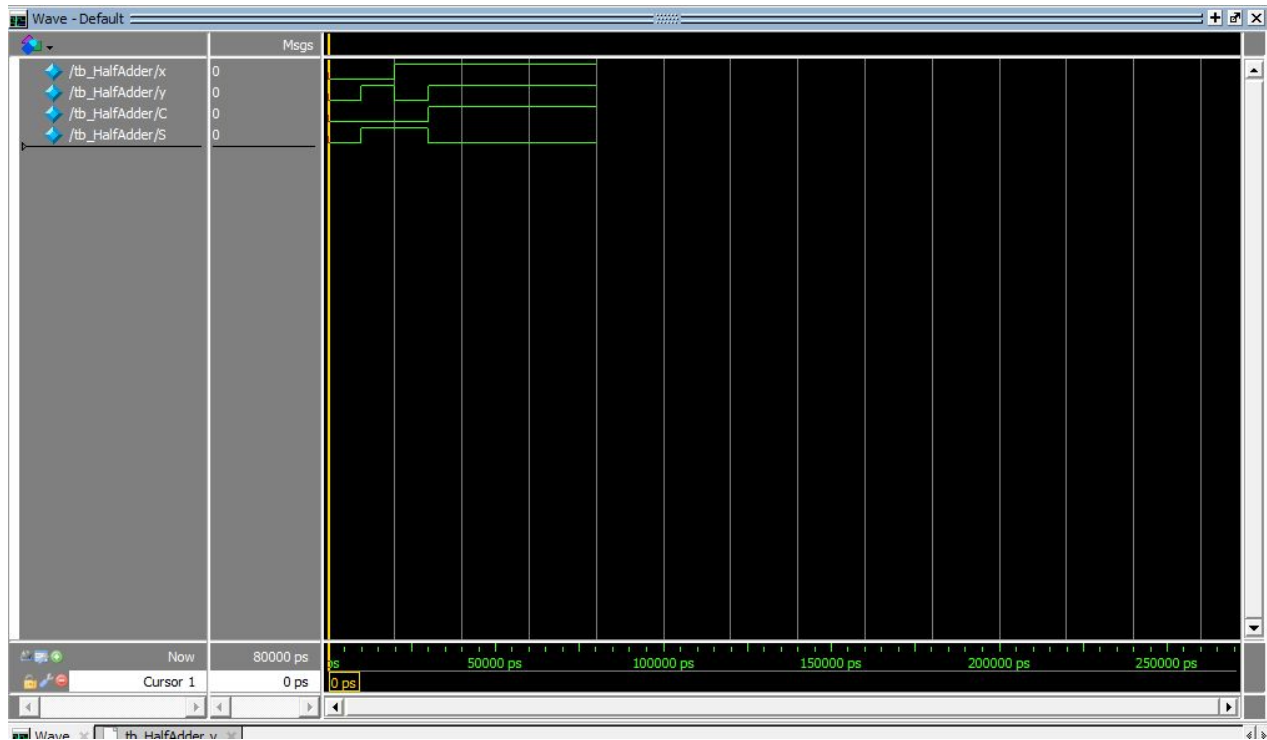



Exercise 2B:

In exercise 2A, that task was to create a full adder circuit and make a testbench for it. First, the truth table and output functions were determined. Second, the Verilog Entry was created based on the functions determined. Third, the test bench file was created, following the steps in Exercise 2B. Fourth, the RTL Simulation was run.

Table 2.1 Truth Table for Full Adder Circuit

INPUT			OUTPUT	
A	B	C_in	S	C_out
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Figure 2.1 K-Maps

S K-Map					C_out K-Map				
A/B C_in	00	01	11	10	A/B C_in	00	01	11	10
0		1		1	0			1	
1	1		1		1		1	1	1
$S = A'B'C_{in} + A'BC_{in}' + AB'C_{in}' + ABC_{in}$ $S = C_{in} \text{ XOR } (A \text{ XOR } B)$					$C_{out} = BC_{in} + AC_{in} + AB$				



Figure 2.1. Design Entry of Full Adder

```
FullAdder.v      tb_FullAdder.v      Compil
1 //German E Felisarta III 16101002 Group 3 M 07:30 AM - 10:30 AM
2
3 module FullAdder(A, B, C_in, S, C_out);
4
5     input A, B, C_in;
6     output S, C_out;
7     wire w1;          // S wires
8     wire w2, w3, w4;  // C_out wires
9
10
11     //S Function
12     xor X1 (w1, A, B);
13     xor X2 (S, C_in, w1);
14
15     //C_out Function
16     and A1 (w2, B, C_in);
17     and A2 (w3, A, C_in);
18     and A3 (w4, A, B);
19
20     //joining gates for C_out
21     or (C_out, w2, w3, w4);
22
23
24
25 endmodule
26
27
28 /*
29
30 FULL ADDER FUNCTIONS
31
32 S = C_in XOR (A XOR B)
33 C_out = BC_in + AC_in + AB
34
35
36 */
37
```



Figure 2.2. RTL View of Full Adder


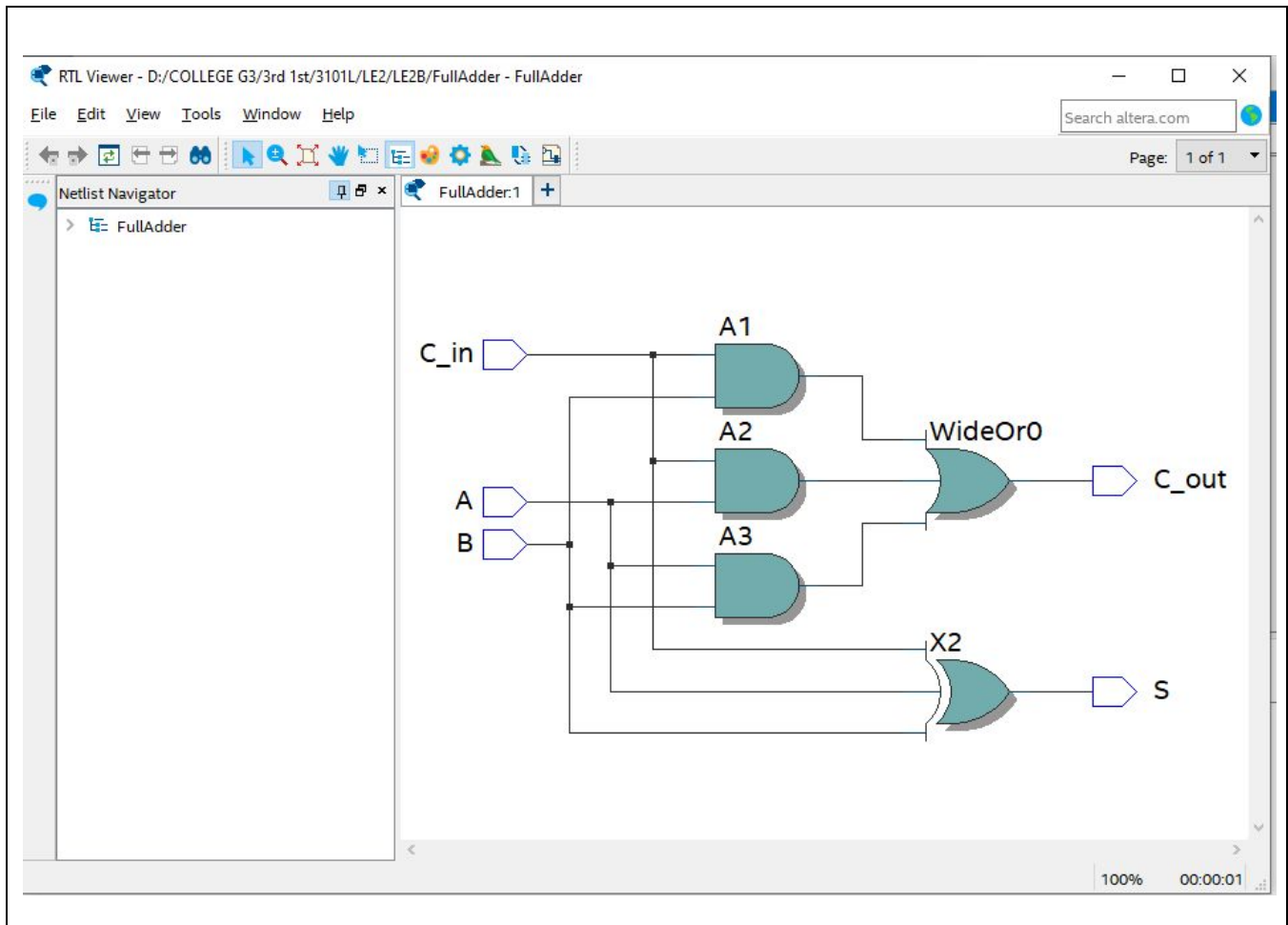


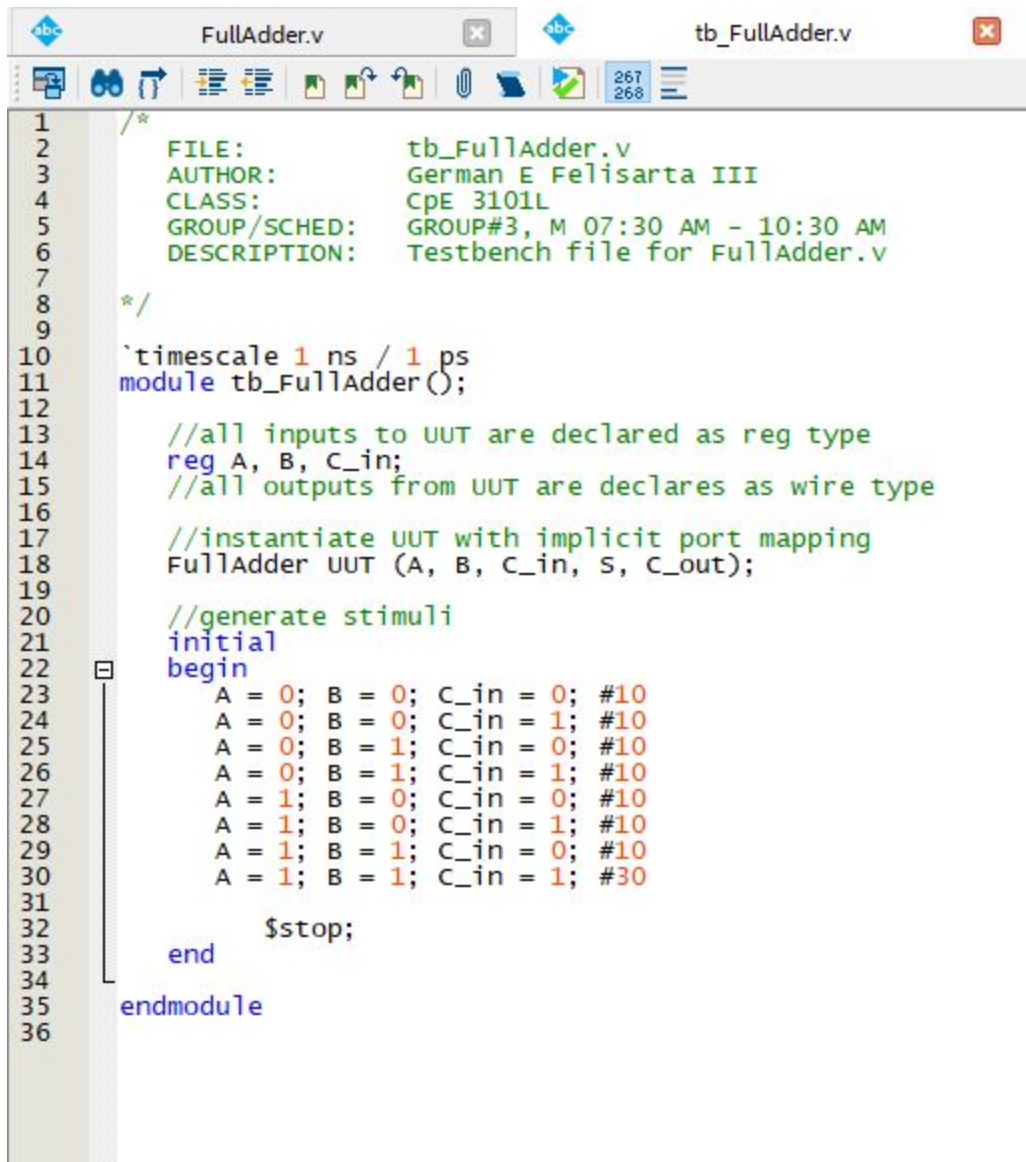

Figure 2.3. Design Entry of Full Adder Testbench



```
1  /*
2  FILE:          tb_FullAdder.v
3  AUTHOR:       German E Felisarta III
4  CLASS:       CpE 3101L
5  GROUP/SCHED: GROUP#3, M 07:30 AM - 10:30 AM
6  DESCRIPTION:  Testbench file for FullAdder.v
7  */
8
9
10 `timescale 1 ns / 1 ps
11 module tb_FullAdder();
12
13     //all inputs to UUT are declared as reg type
14     reg A, B, C_in;
15     //all outputs from UUT are declares as wire type
16
17     //instantiate UUT with implicit port mapping
18     FullAdder UUT (A, B, C_in, S, C_out);
19
20     //generate stimuli
21     initial
22     begin
23         A = 0; B = 0; C_in = 0; #10
24         A = 0; B = 0; C_in = 1; #10
25         A = 0; B = 1; C_in = 0; #10
26         A = 0; B = 1; C_in = 1; #10
27         A = 1; B = 0; C_in = 0; #10
28         A = 1; B = 0; C_in = 1; #10
29         A = 1; B = 1; C_in = 0; #10
30         A = 1; B = 1; C_in = 1; #30
31
32         $stop;
33     end
34 endmodule
35
36
```



Figure 2.4. Flow Summary


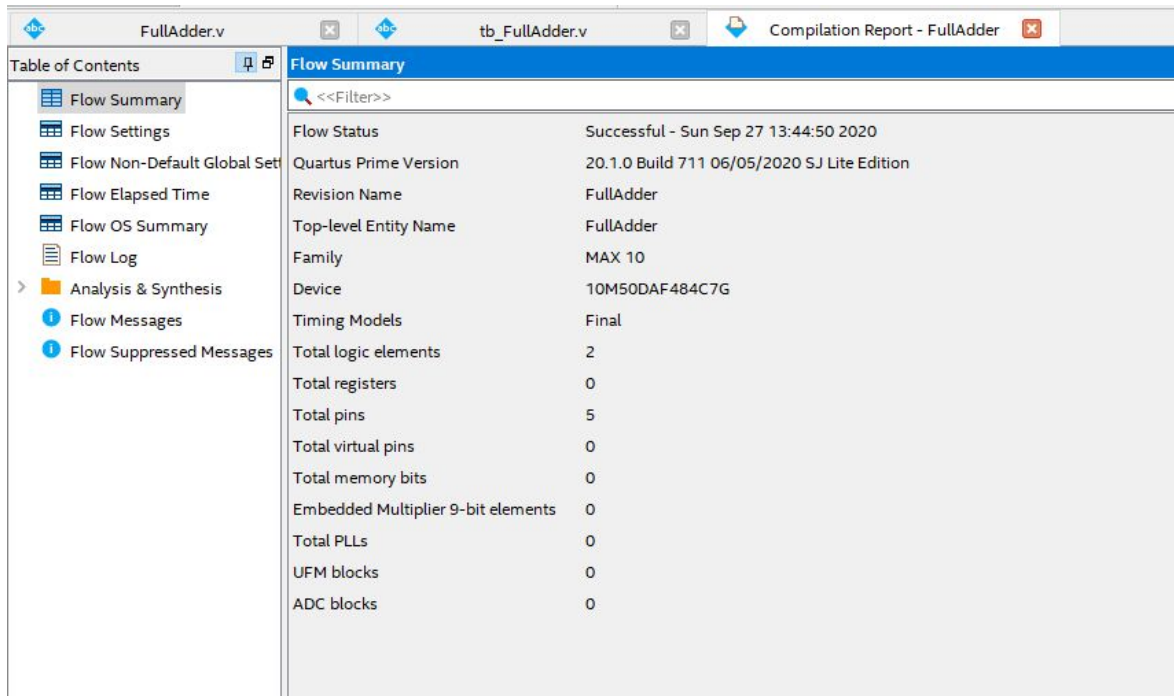


Figure 2.5. Timing Diagram in ModelSim-Altera

 



Exercise 2C:

In exercise 2C, that task was to create a 4 Bit adder circuit using the Full Adder Circuit created in Exercise 2B and make a testbench for it. First, another module called Adder_4Bit was made. Second, the Verilog Entry was based on the schematic diagram in the lab exercise sheet where 4 full adders are connected with the C_Out and C_In ports. Third, the test bench file was created, following the steps in Exercise 2B. Fourth, the RTL Simulation was run.

Figure 3.1. Design Entry of Adder_4Bit

```
1 //German E Felisarta III 16101002 Group 3 M 07:30 AM - 10:30 AM
2
3 module Adder_4Bit(X, Y, CIn, SUM, COut);
4
5     input    [3:0]X;
6     input    [3:0]Y;
7     input    CIn;
8     output   [3:0]SUM;
9     output   COut;
10    wire     w1, w2, w3;
11
12    FullAdder FA1 (X[0], Y[0], CIn, SUM[0], w1);
13    FullAdder FA2 (X[1], Y[1], w1, SUM[1], w2);
14    FullAdder FA3 (X[2], Y[2], w2, SUM[2], w3);
15    FullAdder FA4 (X[3], Y[3], w3, SUM[3], COut);
16
17
18 endmodule
19
20
21 module FullAdder(A, B, C_in, S, C_out);
22
23     input A, B, C_in;
24     output S, C_out;
25     wire w1, w2, w3, w4;
26
27     //S Function
28     xor X1 (w1, A, B);
29     xor X2 (S, C_in, w1);
30
31     //C_out Function
32     and A1 (w2, B, C_in);
33     and A2 (w3, A, C_in);
34     and A3 (w4, A, B);
35
36     //joining gates for C_out
37     or (C_out, w2, w3, w4);
38
39
40
41 endmodule
42
43 <
```




Figure 3.2. RTL View of Adder_4Bit

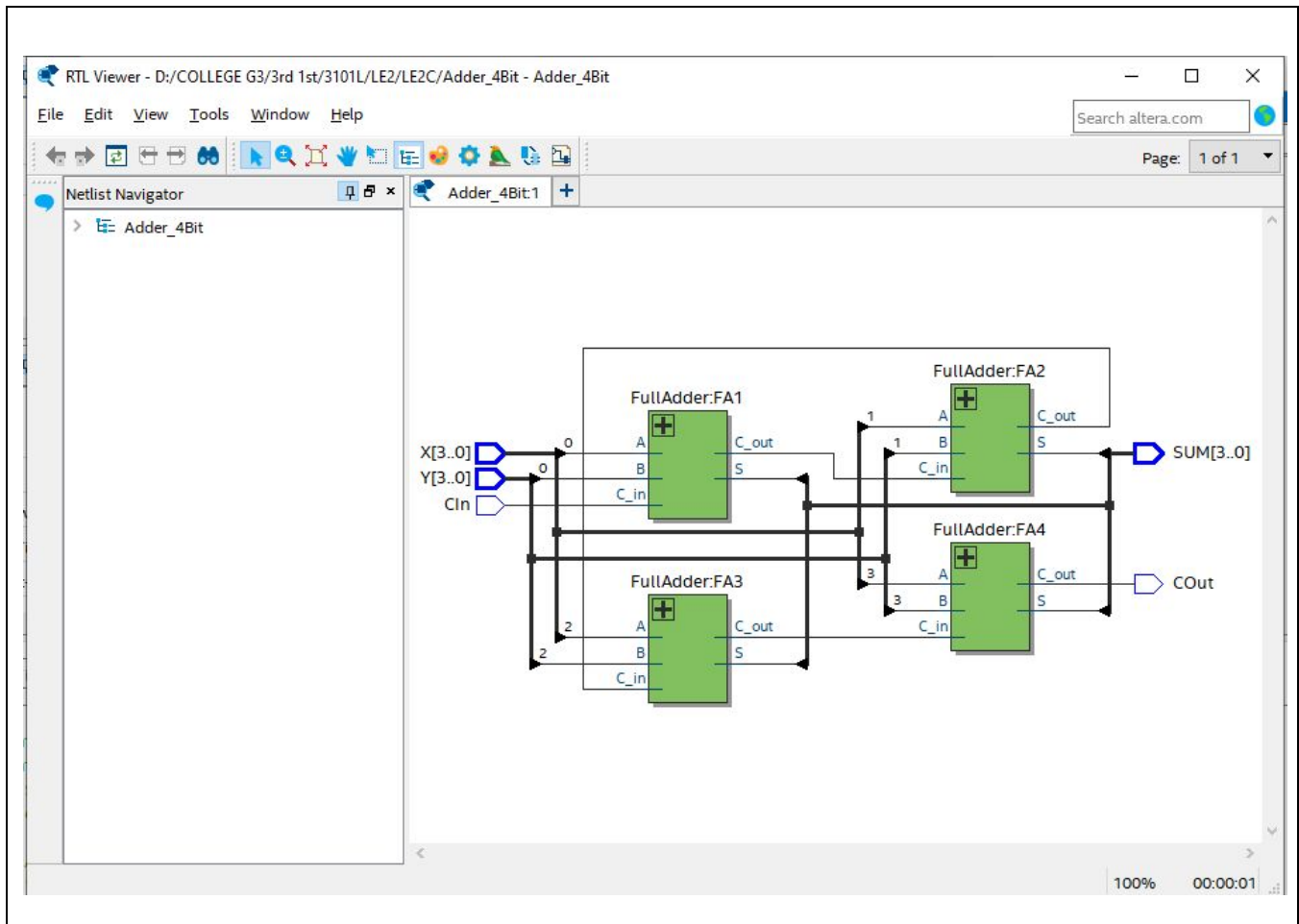




Figure 3.3. Design Entry of Adder_4Bit Testbench

```
1  /*
2  FILE:          tb_Adder_4Bit.v
3  AUTHOR:       German E Felisarta III
4  CLASS:        Cpe 3101L
5  GROUP/SCHED: M 7:30 - 10:30 AM
6  DESC:         Testbench file for Adder_4Bit.v
7
8  */
9  `timescale 1 ns / 1 ps
10 module tb_Adder_4Bit();
11
12     //all inputs to UUT are declared as reg type
13     reg [3:0] A, B;
14     reg      C_in;
15
16     //all outputs from UUT are declared as wire type
17     wire [3:0] S;
18     wire      C_out;
19
20     //instantiate UUT with explicit mapping
21     Adder_4Bit UUT (A, B, C_in, S, C_out);
22
23     //generate stimuli
24     initial
25     begin
26         A = 4'd0;   B = 4'd0;   C_in = 0; #10
27         A = 4'd3;   B = 4'd8;   C_in = 1; #10
28         A = 4'd11;  B = 4'd3;   C_in = 0; #10
29         A = 4'd12;  B = 4'd6;   C_in = 0; #10
30         A = 4'd5;   B = 4'd4;   C_in = 1; #10
31         A = 4'd1;   B = 4'd9;   C_in = 0; #10
32         A = 4'd15;  B = 4'd15;  C_in = 0; #10
33         A = 4'd15;  B = 4'd15;  C_in = 1; #10
34
35         $stop;
36     end
37 endmodule
```



Figure 3.4. Flow Summary

The screenshot shows the Quartus Prime IDE interface. At the top, there are three tabs: 'Adder_4Bit.v', 'Compilation Report - Adder_4Bit', and 'tb_Adder_4Bit.v'. The 'Compilation Report - Adder_4Bit' tab is active, displaying the 'Flow Summary' section. On the left, a 'Table of Contents' pane lists various report sections, with 'Flow Summary' highlighted. The main content area shows a table with the following data:

Flow Summary	
Flow Status	Successful - Sun Sep 27 14:41:28 2020
Quartus Prime Version	20.1.0 Build 711 06/05/2020 SJ Lite Edition
Revision Name	Adder_4Bit
Top-level Entity Name	Adder_4Bit
Family	MAX 10
Device	10M50DCF484C7G
Timing Models	Final
Total logic elements	8
Total registers	0
Total pins	14
Total virtual pins	0
Total memory bits	0
Embedded Multiplier 9-bit elements	0
Total PLLs	0
UFM blocks	0
ADC blocks	0



Figure 3.5. Timing Diagram in ModelSim-Altera

